



Department of Computer Science & Engineering

Experiment-5

Design Verilog HDL to implement Decimal adder.

Aim: To design Verilog HDL code for Decimal adder

Numbers considered: 9 and 8

$$9 + 8 = 17$$

$$1001 + 1000 = 10001$$

The sum 17 is more than 9. So, add 6 to it.

$$17+6 = 23 \text{ (in binary 23 is 10111)}$$

The least significant 4 bits (which is "0111") represent the units digit and the MSB (4th bit which is '1') bit represents the tens digit.

Verilog code:

```
module bcd_adder(a,b,carry_in,sum,carry);
    input [3:0] a,b;
    input carry_in;
    output reg [3:0] sum;
    output reg carry;
    reg [4:0] sum_temp;
    always @(a,b,carry_in)
    begin
        sum_temp = a+b+carry_in;
        if(sum_temp > 9)
            begin
                sum_temp = sum_temp+6;
                carry = 1;
                sum = sum_temp[3:0];
            end
        else
            begin
                carry = 0;
                sum = sum_temp[3:0];
            end
        end
    end
endmodule
```

Testbench for BCD adder:

```
module tb_bcdadder;
    reg [3:0] a;
    reg [3:0] b;
    reg carry_in;
    wire [3:0] sum;
```


Department of Computer Science & Engineering

```

wire carry;
bcd_adder uut ( .a(a), .b(b), .carry_in(carry_in), .sum(sum), .carry(carry));
initial begin
    a = 0; b = 0; carry_in = 0; #100;
    a = 6; b = 9; carry_in = 0; #100;
    a = 3; b = 3; carry_in = 1; #100;
    a = 4; b = 5; carry_in = 0; #100;
    a = 8; b = 2; carry_in = 0; #100;
    a = 9; b = 9; carry_in = 1; #100;
end
endmodule

```

Timing Diagram

 

Result

Verilog HDL code for Decimal adder is designed and simulated.