

## Department of Computer Science & Engineering


### Experiment-7

#### Design Verilog program to implement types of De-Multiplexer

**Aim:** To develop Verilog code to implement types of De-multiplexer.

##### a) 1:2 Demux

**Symbol**

 

**Truth Table**


Input	Outputs	
S	Y1	Y0
0	0	A
1	A	0

**Expression**

$$Y1 = S.A$$

$$Y0 = S'.A$$

**Logic Diagram**

 

**Verilog dataflow description code**


```
module demux_12 (s, a, y0, y1);
input s, a;
output y0, y1;
assign {y0, y1} = s ? {1'b0, a} : {a, 1'b0};
endmodule
```

## Department of Computer Science & Engineering

### Testbench code


```
module demux12_tb;
reg s;
reg a;
wire y0;
wire y1;
demux_12 uut (.s(s), .a(a), .y0(y0), .y1(y1));
initial begin
s = 0; a = 1; #100;
s = 1; a = 1; #100;
end
endmodule
```

### Timing Diagram

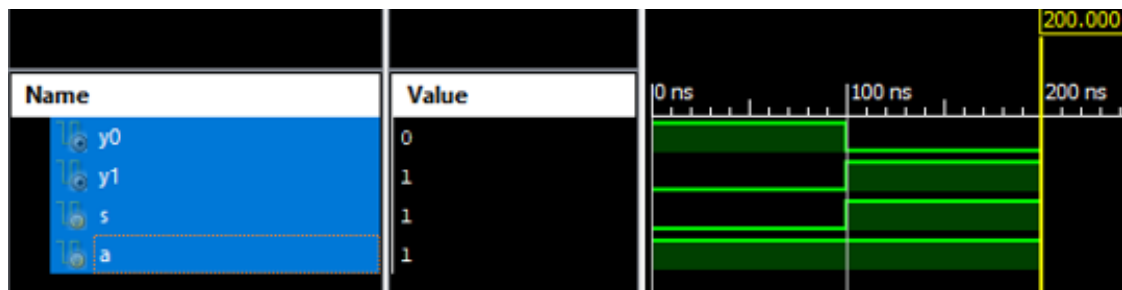

### b) 1:4 Demux

#### Symbol

 

#### Truth Table

Inputs		Outputs			
S <sub>1</sub>	S <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	A
0	1	0	0	A	0
1	0	0	A	0	0
1	1	A	0	0	0

#### Expression

$$Y_0 = S_1' \cdot S_0' \cdot A$$


## Department of Computer Science & Engineering

$$Y_3 = S_1' \cdot S_0 \cdot A$$

$$Y_2 = S_1 \cdot S_0' \cdot A$$

$$Y_1 = S_1 \cdot S_0 \cdot A$$

### Logic Diagram

 

### Verilog behavioral description code

```
module demux_14(s, a, y0, y1, y2, y3);
input [1:0] s;
input a;
output reg y0, y1, y2, y3;
always @ (*)
begin
    case(s)
        2'b00: {y3, y2, y1, y0} = {3'b0, a};
        2'b01: {y3, y2, y1, y0} = {2'b0, a, 1'b0};
        2'b10: {y3, y2, y1, y0} = {1'b0, a, 2'b0};
        2'b11: {y3, y2, y1, y0} = {a, 3'b0};
    endcase
end
endmodule
```


### Testbench code

```
module demux14_tb;
reg [1:0] s;
reg a;
wire y0, y1, y2, y3;
```

## Department of Computer Science & Engineering


```
demux_14 uut(.s(s), .a(a), .y0(y0), .y1(y1), .y2(y2), .y3(y3));
initial begin
s=2'b00; a=1; #100;
s=2'b01; a=1; #100;
s=2'b10; a=1; #100;
s=2'b11; a=1; #100;
end
endmodule
```

### Timing Diagram

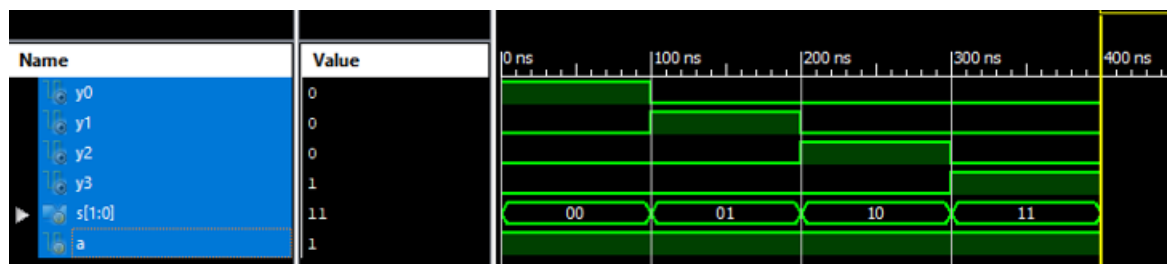

### c) 1:8 Demux

#### Symbol

 

#### Truth Table

Inputs			Outputs							
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	A
0	0	1	0	0	0	0	0	0	A	0
0	1	0	0	0	0	0	0	A	0	0
0	1	1	0	0	0	0	A	0	0	0
1	0	0	0	0	0	A	0	0	0	0
1	0	1	0	0	A	0	0	0	0	0
1	1	0	0	A	0	0	0	0	0	0
1	1	1	A	0	0	0	0	0	0	0

## Department of Computer Science & Engineering

### Expression

$$Y_0 = S_2' \cdot S_1' \cdot S_0' \cdot A$$

$$Y_1 = S_2' \cdot S_1' \cdot S_0 \cdot A$$

$$Y_2 = S_2' \cdot S_1 \cdot S_0' \cdot A$$

$$Y_3 = S_2' \cdot S_1 \cdot S_0 \cdot A$$


$$Y_4 = S_2 \cdot S_1' \cdot S_0' \cdot A$$

$$Y_5 = S_2 \cdot S_1' \cdot S_0 \cdot A$$

$$Y_6 = S_2 \cdot S_1 \cdot S_0' \cdot A$$

$$Y_7 = S_2 \cdot S_1 \cdot S_0 \cdot A$$

### Logic Diagram

 

### Verilog behavioral description code

```
module demux_18(s, a, y);
input [2:0] s;
input a;
output reg [7:0] y;
always @ (*)
```



# A T M E

College of Engineering




## Department of Computer Science & Engineering

```
begin
case (s)
3'b000: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={7'b0, a};
3'b001: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={6'b0, a, 1'b0};
3'b010: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={5'b0, a, 2'b0};
3'b011: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={4'b0, a, 3'b0};
3'b100: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={3'b0, a, 4'b0};
3'b101: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={2'b0, a, 5'b0};
3'b110: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={1'b0, a, 6'b0 };
3'b111: {y[7], y[6], y[5], y[4], y[3], y[2], y[1], y[0]}={a, 7'b0};
endcase
end
endmodule
```

### Testbench code

```
module demux18_tb;
reg [2:0] s;
reg a;
wire [7:0] y;
demux_18 uut(.s(s), .a(a), .y(y));
initial begin
s=3'b000; a=1; #100;
s=3'b001; a=1; #100;
s=3'b010; a=1; #100;
s=3'b011; a=1; #100;
s=3'b100; a=1; #100;
s=3'b101; a=1; #100;
s=3'b110; a=1; #100;
s=3'b111; a=1; #100;
end
endmodule
```

### Timing Diagram

 

### Result

Verilog programs are developed to implement types of De-Multiplexer.