

Department of Computer Science & Engineering


Experiment-8

Design Verilog program for implementing various types of Flip-Flops such as SR, JK and D.

Aim: To develop Verilog code to implement types of flip-flops.

a) SR Flip-flop


Symbol

 

Truth table

INPUTS			OUTPUTS		ACTIONS
CLK	S	R	Q _{n+1}	Q _{n+1}	
1	0	0	Q _n	Q _n	No Change
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	X	X	Indeterminate

Logic Diagram

 

Verilog code

```

module sr_ff(s, r, clk, q, qb);
input s, r, clk;
output reg q, qb;
always@(posedge clk)
begin
case({s,r})
2'b00: begin q = q; qb=qb; end
2'b01: begin q = 1'b0; qb=1'b1; end
2'b10: begin q = 1'b1; qb=1'b0; end
2'b11: begin q = 1'bx; qb=1'bx; end
endcase
end
endmodule

```



A T M E

College of Engineering




Department of Computer Science & Engineering

Testbench code


```
module sr_tb;
  reg s,r,clk;
  wire q,qb;
  sr_ff uut(.s(s), .r(r), .clk(.clk), .q(q), .qb(qb));
  initial begin
    clk=0;
    forever #50 clk=~clk;
  end
  initial begin
    s=0; r=1; #100;
    s=0; r=0; #100;
    s=1; r=0; #100;
    s=1; r=1; #100;
    $finish();
  end
end
endmodule
```

Timing Diagram

 

b) JK Flip-flop

Symbol

 


Truth table

Clock	J	K	Q_{n+1}	State
0	x	x	Q_n	
1	0	0	Q_n	Hold
1	0	1	0	Reset
1	1	1	1	Set
1	1	1	$\overline{Q_n}$	Toggle

Department of Computer Science & Engineering

Logic Diagram

 

Verilog code


```
module jk_ff (j, k, clk, q, qb);
input j, k, clk;
output reg q, qb;
always @ (posedge clk)
begin
    case ({j,k})
        2'b00 : begin q = q; qb=qb; end
        2'b01 : begin q = 1'b0; qb=1'b1; end
        2'b10 : begin q = 1'b1; qb=1'b0; end
        2'b11 : begin q = ~q; qb=~qb; end
    endcase
endmodule
```

Testbench code

```
module jk_tb;
reg j, k, clk;
wire q, qb;
jk_ff uut(.j(j), .k(k), .clk(.clk), .q(q), .qb(qb));
initial begin
    clk=0;
    forever #50 clk=~clk;
end
initial begin
    j=0; k=1; #100;
    j=0; k=0; #100;
    j=1; k=0; #100;
    j=1; k=1; #100;
    $finish();
end
endmodule
```


Department of Computer Science & Engineering

Timing Diagram

 

c) D Flip-flop


Symbol

 

Truth table

CLK	Input D	Output Q _{n+1}
1	0	0
1	1	1
0	X	No Change

Logic Diagram

 

Verilog code

```

module d_ff(clk, d, q, qb);
input clk, d;
output reg q;
always @ (posedge clk)
begin
q = d; qb=~q;
end
endmodule

```



A T M E

College of Engineering




Department of Computer Science & Engineering

Testbench code

```
module d_tb;
reg d, clk;
wire q, qb;
d_ff UUT(.d(d), .clk(clk), .q(q), .qb(qb));
initial begin
    clk = 0;
    forever #50 clk=~clk;
end
initial begin
    d = 1'b0; #100
    d = 1'b1; #100
    $finish();
end
endmodule
```

Timing Diagram

 

Result

Verilog programs for implementing SR flip-flop, JK flip-flop and D flip-flop are developed.