

## Department of Computer Science & Engineering


### Experiment-4

**Design Verilog HDL to implement Binary Adder-Subtractor- Half and full adder, Half and full subtractor.**

**Aim:** To Design Verilog HDL to implement Half adder, full adder, Half subtractor and full subtractor.

#### a. Half Adder

**Symbol**

 

**Truth table**


INPUT		OUTPUT	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

**Expression**

$$S = A'B + AB' = A \oplus B$$

$$C = AB$$

**Logic diagram**

 

Circuit Diagram

**Verilog code**


```
module half_adder (a,b,s,c);
input a,b;
output s,c;
assign s= a ^ b;
assign c= a & b;
endmodule
```

## Department of Computer Science & Engineering

### Testbench code


```
module half_adder_tb;
reg a,b;
wire s,c;
half_adder uut (.a(a),.b(b),.s(s),.c(c));
initial begin
a = 0; b = 0;
#100
a = 0; b = 1;
#100
a = 1; b = 0;
#100
a = 1; b = 1;
#100
$finish();
end
endmodule
```

### Timing Diagram

 

### b. Full Adder

#### Symbol

 

#### Truth table

INPUT			OUTPUT	
A	B	Cin	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


## Department of Computer Science & Engineering

### Expression

$$S = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = (A \& B) \vee (B \& \text{Cin}) \vee (\text{Cin} \& A)$$

### Logic Diagram

 

### Verilog code


```
module full_adder (a,b,cin,s,count);
input cin, a, b;
output s, count;
assign s = a ^ b ^ cin;
assign count = (a & b) | (b & cin) | (cin & a);
endmodule
```

### Testbench code


```
module full_adder_tb;
reg a,b,cin;
wire s,count;
full_adder uut(.a(a),.b(b),.cin(cin),.s(s),.count(count));
initial begin
a = 0; b = 0; cin = 0;
#100
a = 0; b = 0; cin = 1;
#100
a = 0; b = 1; cin = 0;
#100
a = 0; b = 1; cin = 1;
#100
a = 1; b = 0; cin = 0;
#100
a = 1; b = 0; cin = 1;
#100
a = 1; b = 1; cin = 0;
#100
a = 1; b = 1; cin = 1;
#100
$finish();
end
```

## Department of Computer Science & Engineering

### Timing Diagram

 

### c. Half Subtractor Symbol

 

### Truth table


INPUT		OUTPUT	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### Expression

$$\text{Diff} = A'B + AB' = A \oplus B$$

$$\text{Borrow} = A'B$$

### Logic Diagram

 

### Verilog Code

```

module half_sub( a, b, diff, borrow );
input a, b;
output diff, borrow;
assign diff=a^b;
assign borrow=(~a)&b;
endmodule

```

### Testbench code

```


module half_sub_tb;
reg a,b;
wire diff,borrow;

```


## Department of Computer Science & Engineering

```
half_sub uut (.a(a),.b(b),.diff(diff),.borrow(borrow));
initial begin
a = 0; b = 0;
#100
a = 0; b = 1;
#100
a = 1; b = 0;
#100
a = 1; b = 1;
#100
$finish();
end
endmodule
```

### Timing Diagram

 

### d. Full Subtractor Symbol

 

### Truth table

A	B	B <sub>in</sub>	D	B <sub>out</sub>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


## Department of Computer Science & Engineering

### Expression

$$D = A \oplus B \oplus \text{Bin}$$

$$\text{Bout} = A' \text{Bin} + A' B + B \text{Bin}$$

### Logic Diagram

 

### Verilog code

```
module full_sub(a, b, bin, d, bout);
input a, b, bin;
output d, bout;
assign d = a^b^bin;
assign bout= ((~a) & bin) | ((~a) & b) | (b & bin);
endmodule
```

### Testbench code

```
module full_sub_tb;
reg a,b,bin;
wire d,bout;
full_sub uut(.a(a),.b(b),.bin(bin),.d(d),.bout(bout));
initial begin
a = 0; b = 0; bin = 0;
#100
a = 0; b = 0; bin = 1;
#100
a = 0; b = 1; bin = 0;
#100
a = 0; b = 1; bin = 1;
#100
a = 1; b = 0; bin = 0;
#100
a = 1; b = 0; bin = 1;
#100
a = 1; b = 1; bin = 0;
#100
a = 1; b = 1; bin = 1;
#100
$finish();
end
```




# A T M E

College of Engineering



## Department of Computer Science & Engineering

### Timing Diagram

 

### Result

Verilog HDL code for Half adder, full adder, half subtractor and full subtractor is designed and simulated.