

## Department of Computer Science & Engineering


### Experiment-6

**Design Verilog program to implement Different types of multiplexers like 2:1, 4:1 and 8:1.**

**Aim:** To design Verilog HDL code to implement 2:1, 4:1 and 8:1 multiplexer.

#### a) 2:1 Multiplexer

**Symbol**

 


**Truth table**

Input (S)	Output (Y)
0	I <sub>0</sub>
1	I <sub>1</sub>

**Expression**

$$Y = S' \cdot I_0 + S \cdot I_1$$

**Logic Diagram**

 

**Verilog Dataflow description code**

```
module mux_21(s, i0, i1, y);
input s, i0, i1;
output y;
assign y = s ? i1 : i0;    // or   y=((~select) & i0) | (Select & i1);
endmodule
```

## Department of Computer Science & Engineering

### Testbench code


```
module mux21_tb;
  reg s, i0, i1;
  wire y;
  mux_21 uut(.s(s), .i0(i0), .i1(i1), .y(y));
  initial begin
    s=0; i0=1; i1=0; #100;
    s=1; i0=1; i1=0; #100;
  end
endmodule
```

### Timing Diagram



### b) 4:1 Multiplexer

#### Symbol

 


#### Truth table

Inputs		Output
S1	S0	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

#### Expression

$$Y = S1' S0' I0 + S1' S0 I1 + S1 S0' I2 + S1 S0 I3$$

#### Logic Diagram

 



## Department of Computer Science & Engineering


### Verilog Behavioral Description Code

```
module mux_41 (select, i0, i1, i2, i3, y);
input [1:0] select;
input i0, i1, i2, i3;
output reg y;
always @ (*)
begin
case (select)
2'b00 : y=i0;
2'b01 : y=i1;
2'b10 : y=i2;
2'b11 : y=i3;
endcase
end
endmodule
```

### Test bench code

```
module mux41_tb;
reg [1:0] select;
reg i0, i1, i2, i3;
wire y;
mux_41 uut (.select(select), .i0(i0), .i1(i1), .i2(i2), .i3(i3), .y(y));
initial begin
select=2'b00; i0=0; i1=1; i3=0; i4=1; #100;
select=2'b01; i0=0; i1=1; i3=0; i4=1; #100;
select=2'b10; i0=0; i1=1; i3=0; i4=1; #100;
select=2'b11; i0=0; i1=1; i3=0; i4=1; #100;
end
endmodule
```


### Timing Diagram

 

## Department of Computer Science & Engineering

### c) 8:1 Multiplexer

#### Symbol

 

#### Truth table

Input			Output
S2	S1	S0	y
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

#### Expression

$$Y = S_0' S_1' S_2' I_0 + S_0' S_1' S_2 I_1 + S_0' S_1 S_2' I_2 + S_0' S_1 S_2 I_3 + S_0 S_1' S_2' I_4 + S_0 S_1' S_2 I_5 + S_0 S_1 S_2' I_6 + S_0 S_1 S_2 I_7$$

#### Verilog Behavioral description code

```

module mux_8l(select, i, y);
    input [7:0] i;
    input [2:0] select;
    output reg y;
    always @ (*)
    begin
        case(select)
            3'b000: y=i[0];
            3'b001: y=i[1];
            3'b010: y=i[2];
            3'b011: y=i[3];
            3'b100: y=i[4];
            3'b101: y=i[5];
        endcase
    end
endmodule
    
```

## Department of Computer Science & Engineering

```

3'b110: y=i[6];
3'b111: y=i[7];
endcase
end
endmodule

```


### Testbench code

```

module mux81_tb;
reg [7:0] i;
reg [2:0] select;
wire y;
mux_81 uut (.select(select), .i(i), .y(y));
initial begin
select=3'b000; i=8'b01101010; #100;
select=3'b001; i=8'b01101010; #100;
select=3'b010; i=8'b01101010; #100;
select=3'b011; i=8'b01101010; #100;
select=3'b100; i=8'b01101010; #100;
select=3'b101; i=8'b01101010; #100;
select=3'b110; i=8'b01101010; #100;
select=3'b111; i=8'b01101010; #100;
end
endmodule

```


### Logic diagram

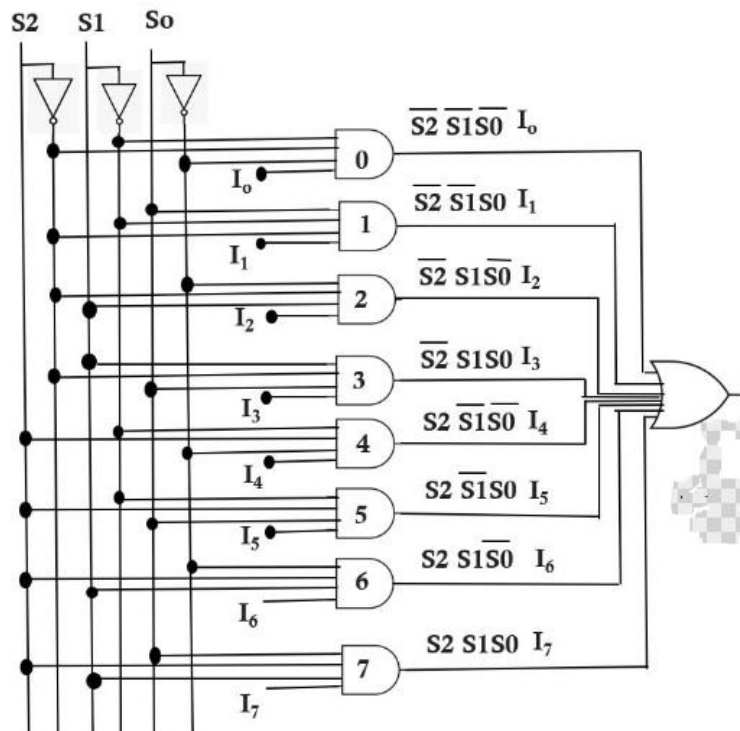



## Department of Computer Science & Engineering

### Timing Diagram

 

### Result

Verilog code for different types of multiplexer are designed and simulated.